

**Grid integration of
offshore wind farms
using HVDC links:
HVDC-VSC technology
overview**

**ICREPQ 2013, Basque Country,
22nd March 2013**

Salvador Ceballos

Salvador.cebillos@tecnalia.com



Introduction

OWPP layouts

HVDC-VSC technology overview

- Two level converters.
- Three level NPC converters
- Modular multilevel converters

Conclusions

Introduction


Transmission layouts for OWPP

HVDC-VSC technology overview

- Two level converters.
- Three level NPC converters
- Modular multilevel converters


Conclusions

Introduction

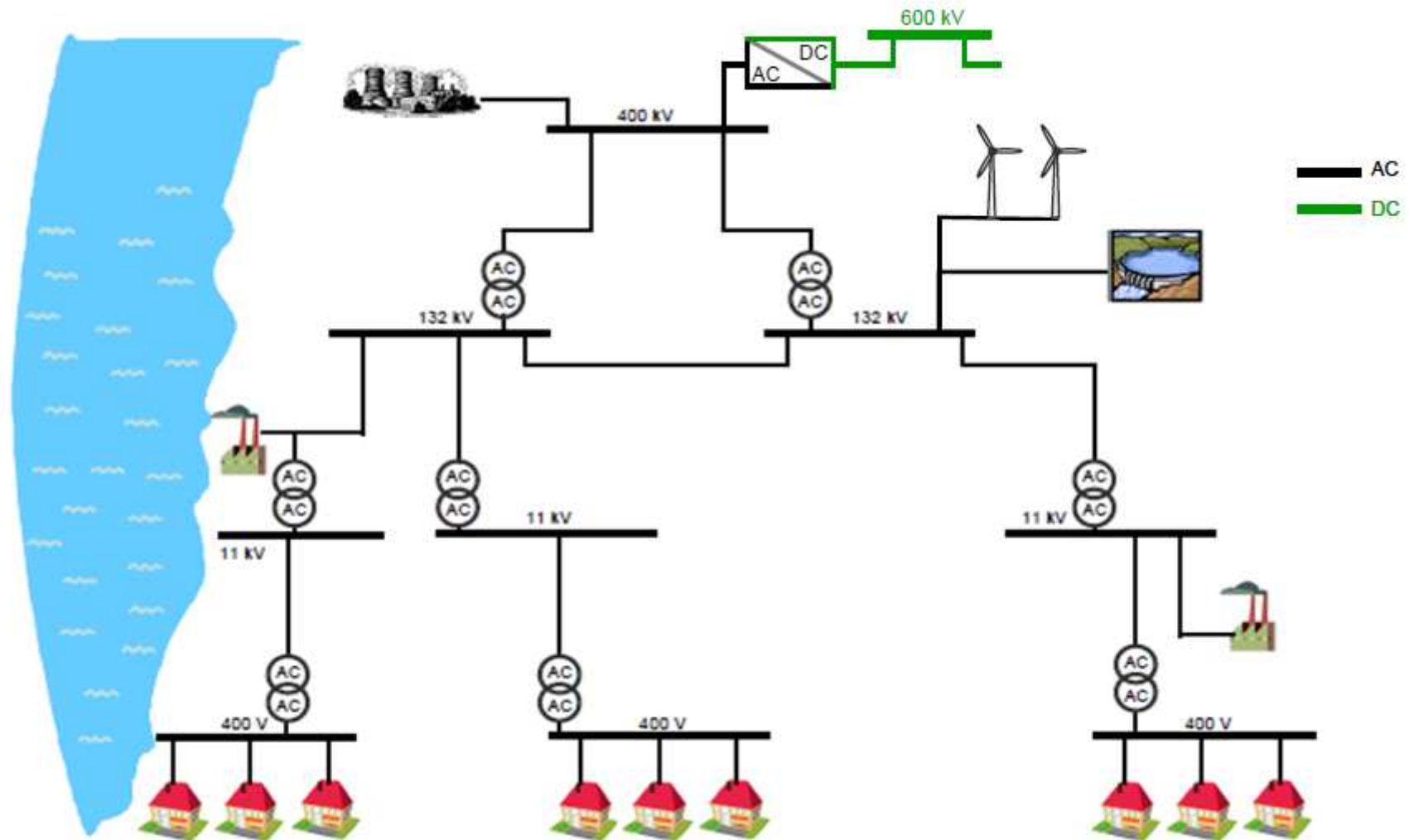

Courtesy of ALSTOM

Introduction

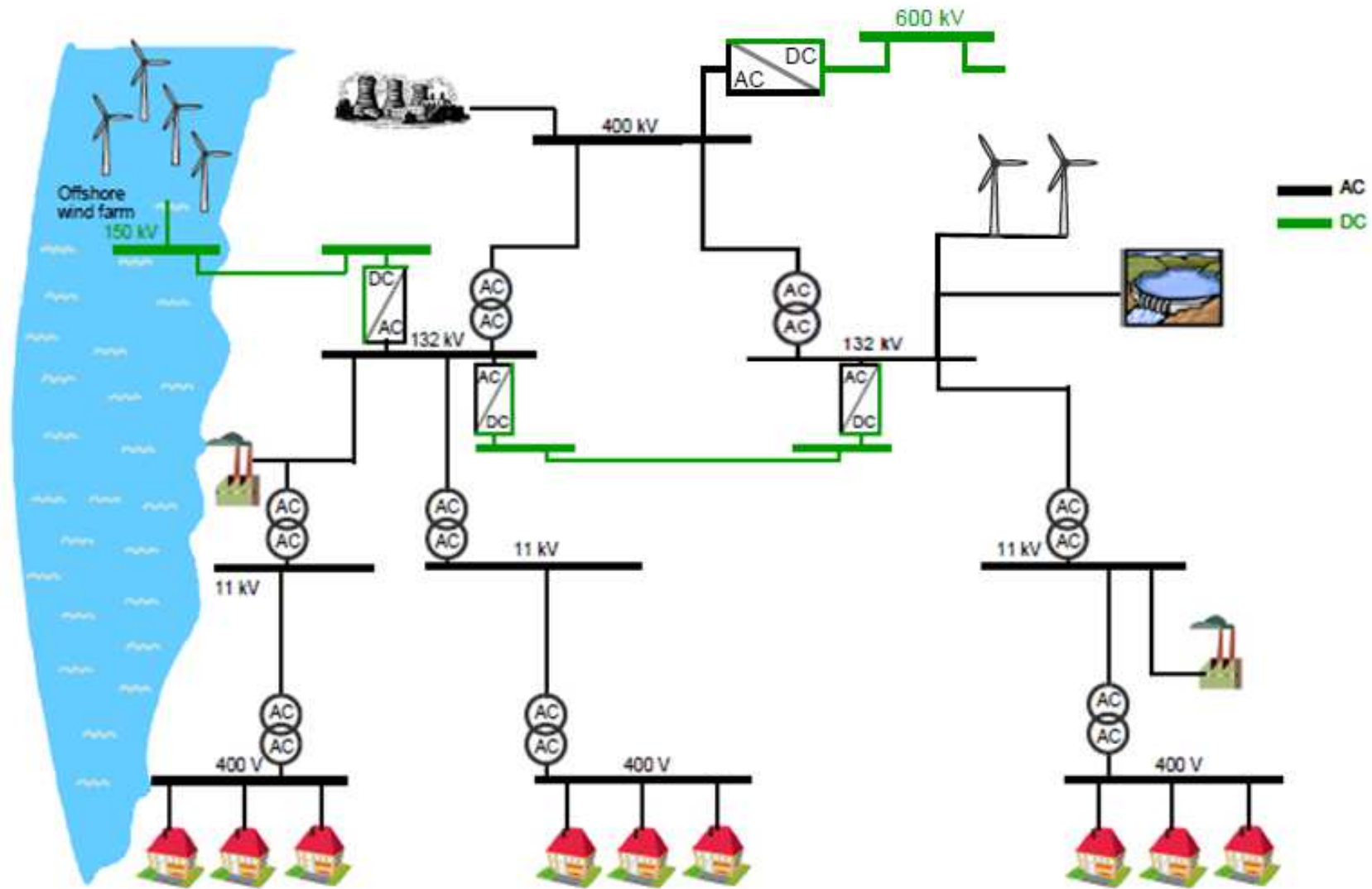

Courtesy of ALSTOM

Introduction


OWPP layouts

HVDC-VSC technology overview

- Two level converters.
- Three level NPC converters
- Modular multilevel converters

Conclusions

OWPP layouts

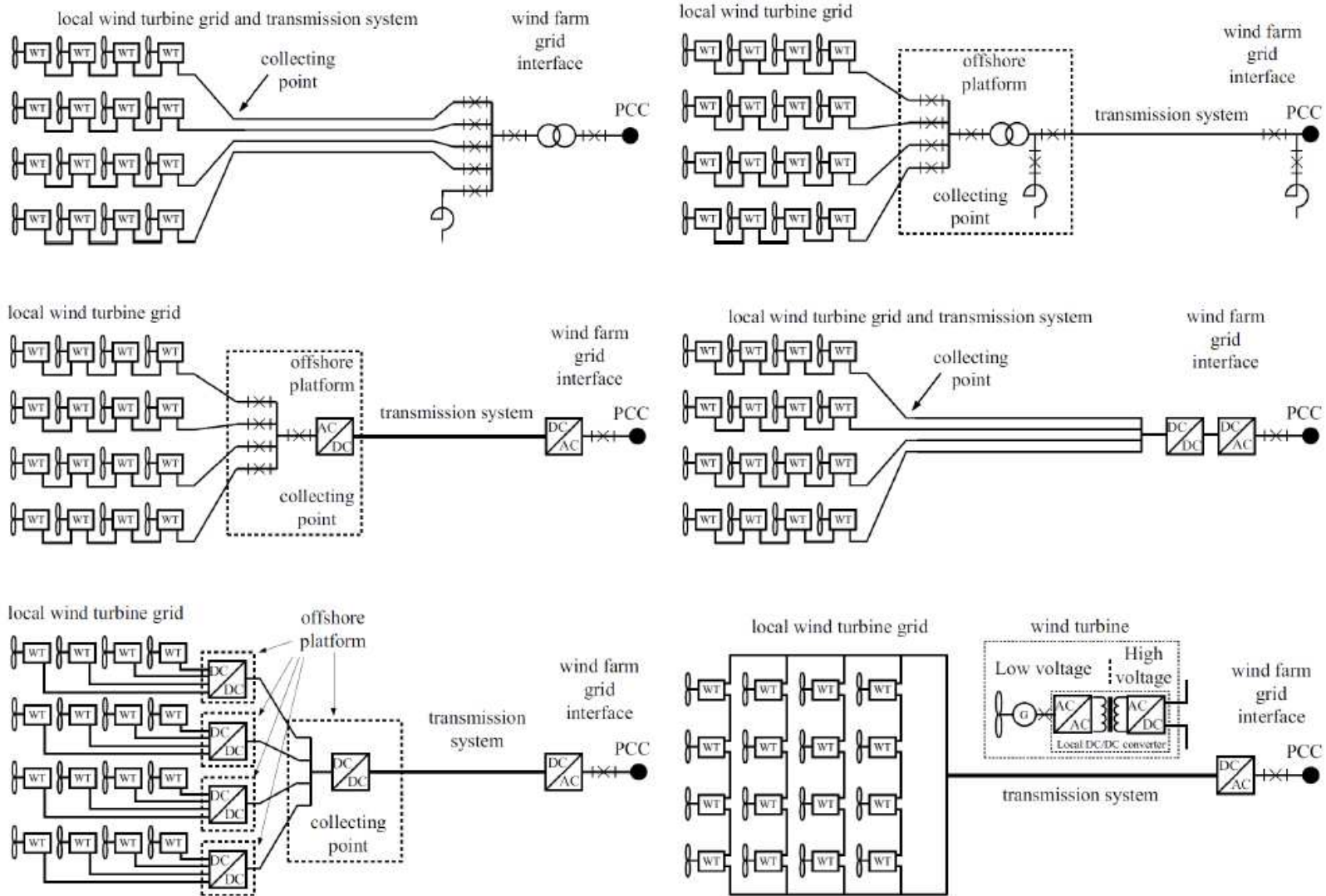


Courtesy of S. Lundberg, "Evaluation of wind farm layouts," *Proceedings of Nordic Workshop on Power and Industrial Electronics*, Trondheim, Norway: NTNU, Department of Electrical Power Engineering, June 2004.

OWPP layouts

■ Small AC layout

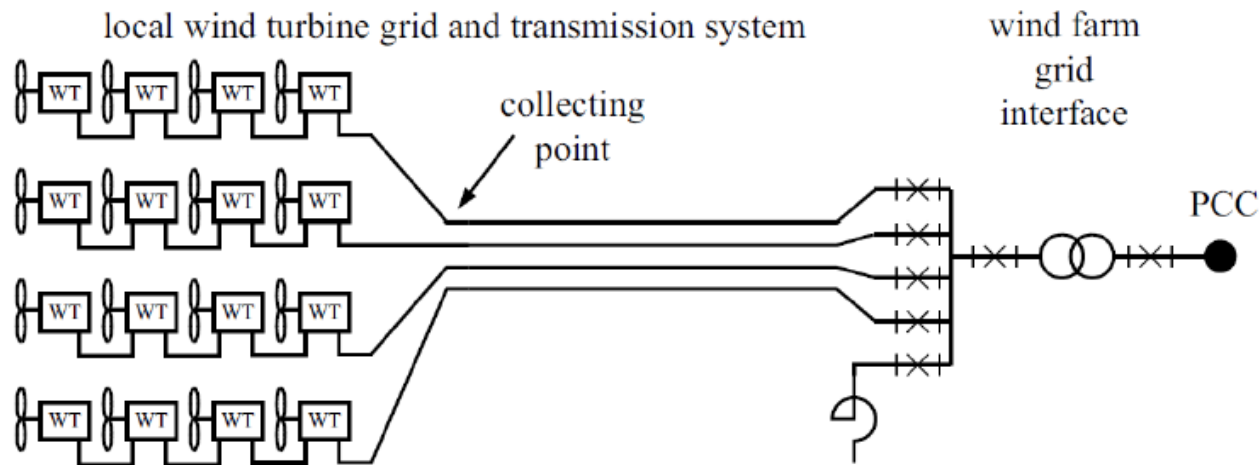- MV AC collector system
- Collector system used to transmit the power to the Point of Common Coupling (PCC) located onshore
- No need of offshore substation
- Unfeasible for large wind farms




Courtesy of S. Lundberg, "Evaluation of wind farm layouts," *Proceedings of Nordic Workshop on Power and Industrial Electronics*, Trondheim, Norway: NTNU, Department of Electrical Power Engineering, June 2004.

OWPP layouts

■ Large AC layout


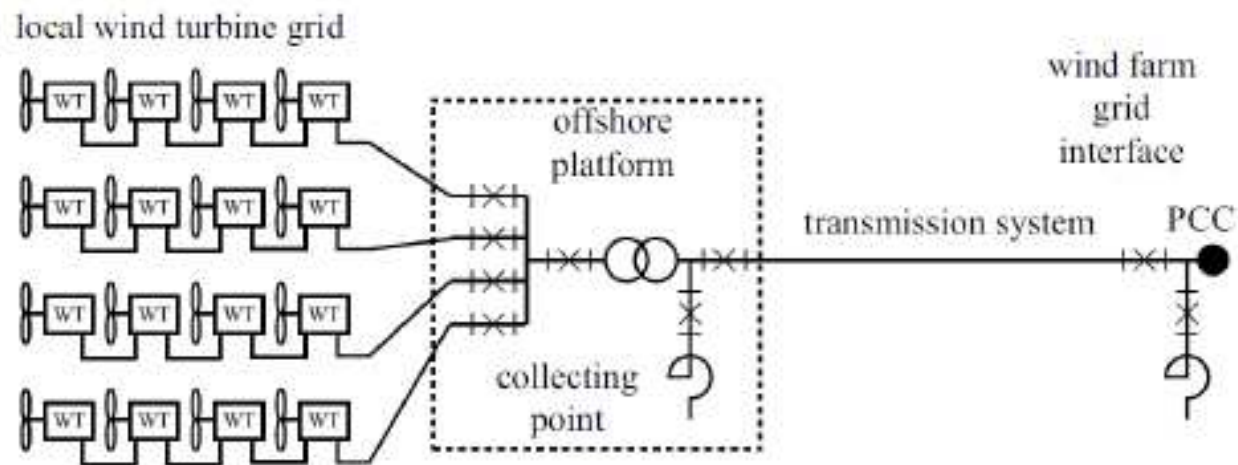
- MV AC collector system
- Offshore platform including transformer, Gas Insulated Switchgear (GIS) and reactive compensation
- HV AC transmission cable
- Onshore station



OWPP layouts

■ Large AC layout. Reactive energy

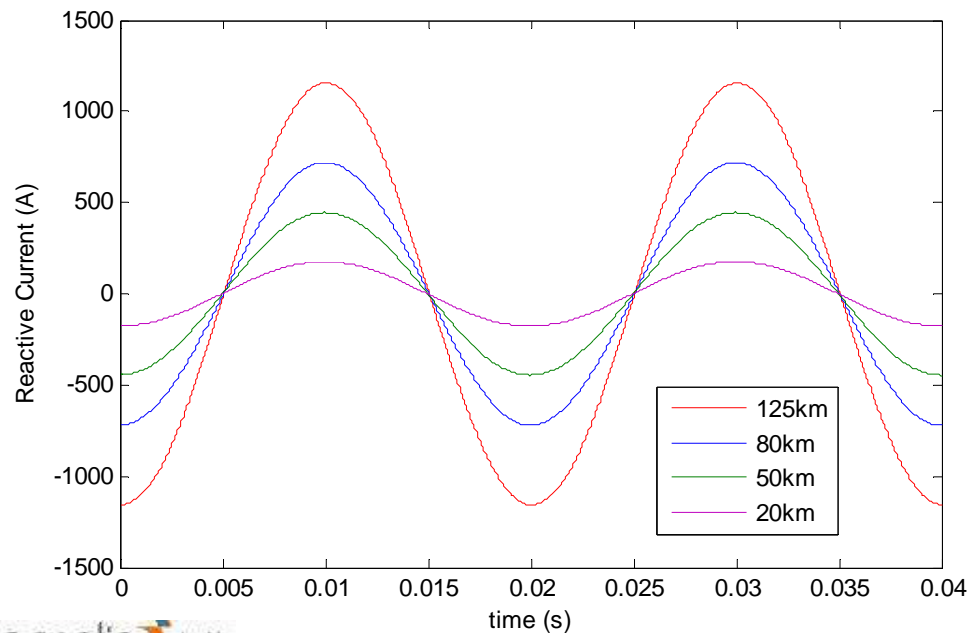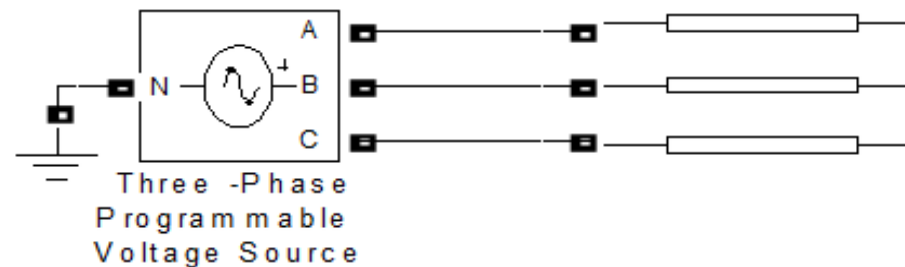- Simulation of a 150 kV submarine cable with no load



The reactive current due to the parasitic cable capacitance increases with the length of the cable. This implies higher losses and a decrease in the active power transmission capacity.


When the cable length is around 125 km the reactive current in the cable is equal to the nominal current!!! It is not possible to transmit active power.

OWPP layouts

■ Large AC layout. Reactive energy

- Simulation of a 150 kV submarine cable with no load


Cross-section of conductor	Diameter of conductor	Insulation thickness	Diameter over insulation	Cross section of screen	Outer diameter of cable	Cable weight (Aluminium)	Cable weight (Copper)	Capacitance	Charging current per phase at 50 Hz	Inductance
mm ²	mm	mm	mm	mm ²	mm	kg/m	kg/m	μF/km	A/km	mH/km
630	29.8	17.0	66.6	2.5	194.0	57.8	69.7	0.19	5.3	0.38
800	33.7	17.0	70.5	2.7	204.0	64.7	79.8	0.21	5.7	0.37
1000	37.9	17.0	75.3	2.8	215.0	71.6	90.5	0.23	6.3	0.36

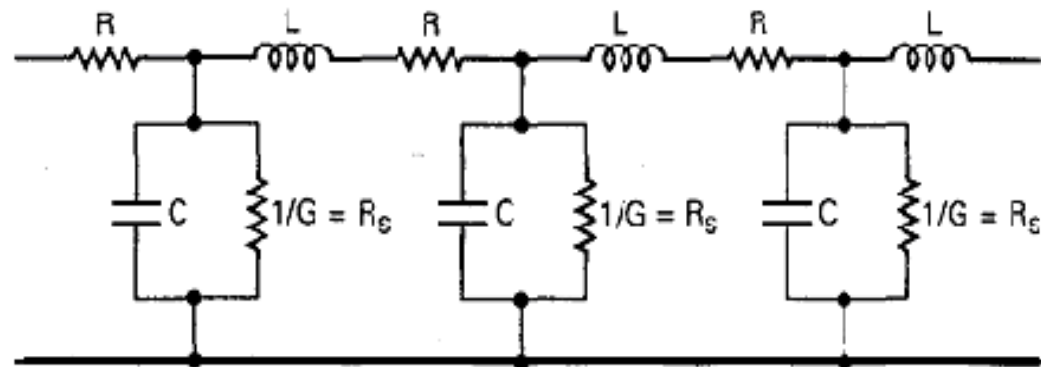

OWPP layouts

■ Large AC layout

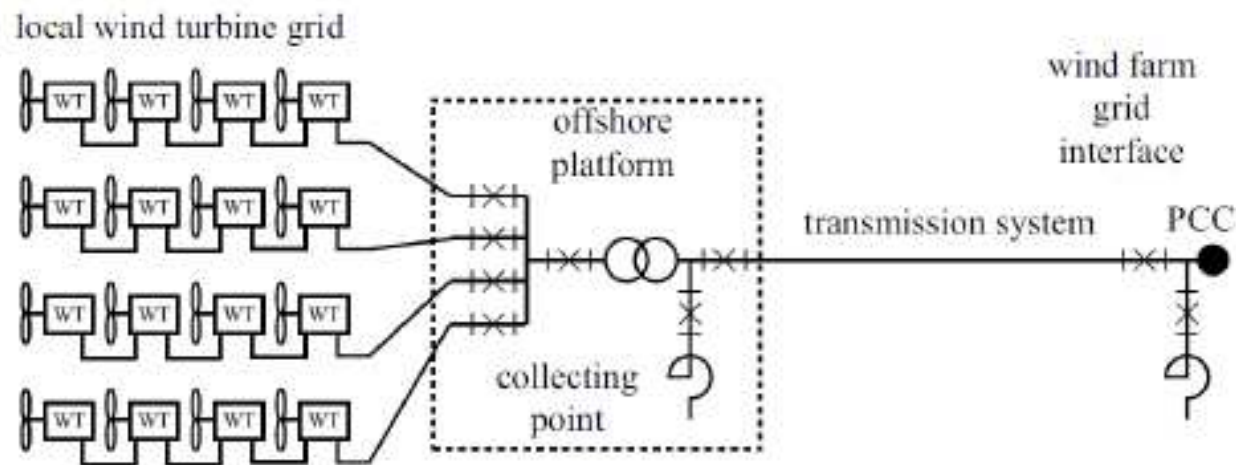
When the transmission cable is longer than 70 km aprox. the reactive current flowing in the cable due to the parasitic capacitance is high enough to reduce considerably its capacity to transmit active power. Therefore this layout is not suitable for those offshore wind farm located far from the PCC.



OWPP layouts

■ HVDC layout

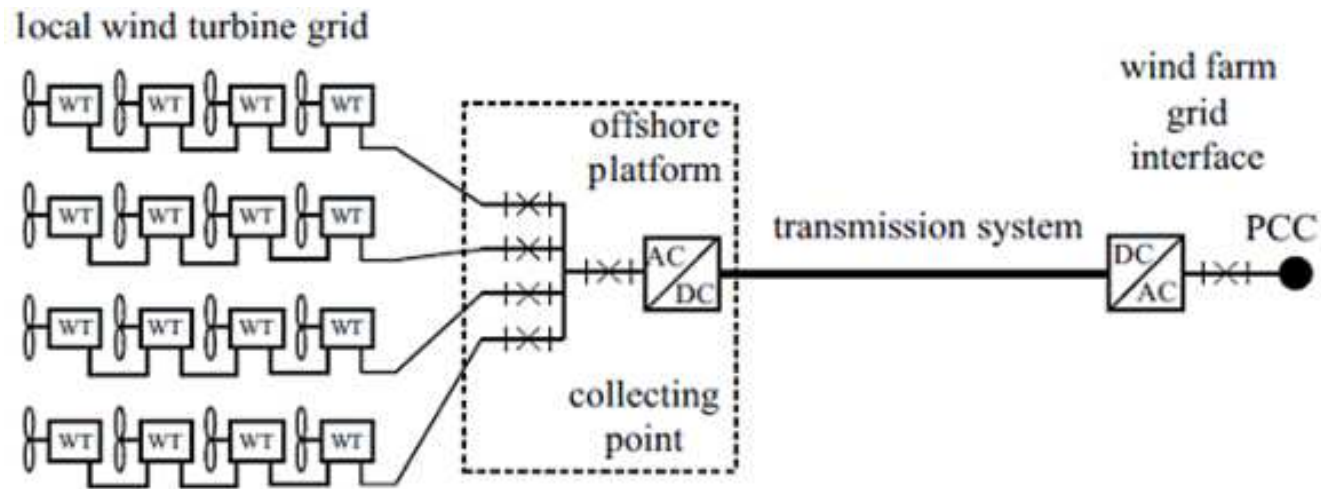- MV AC collector system
- Offshore platform including AC/DC converters
- DC transmission cable
- Onshore station with DC/AC converters



Introduction

OWPP layouts

HVDC-VSC technology overview


- Two level converters.
- Three level NPC converters
- Modular multilevel converters

Conclusions

HVDC-VSC technology overview

■ Two level converters with series connected IGBTs

- ABB late 90s, Siemens 2000-2003


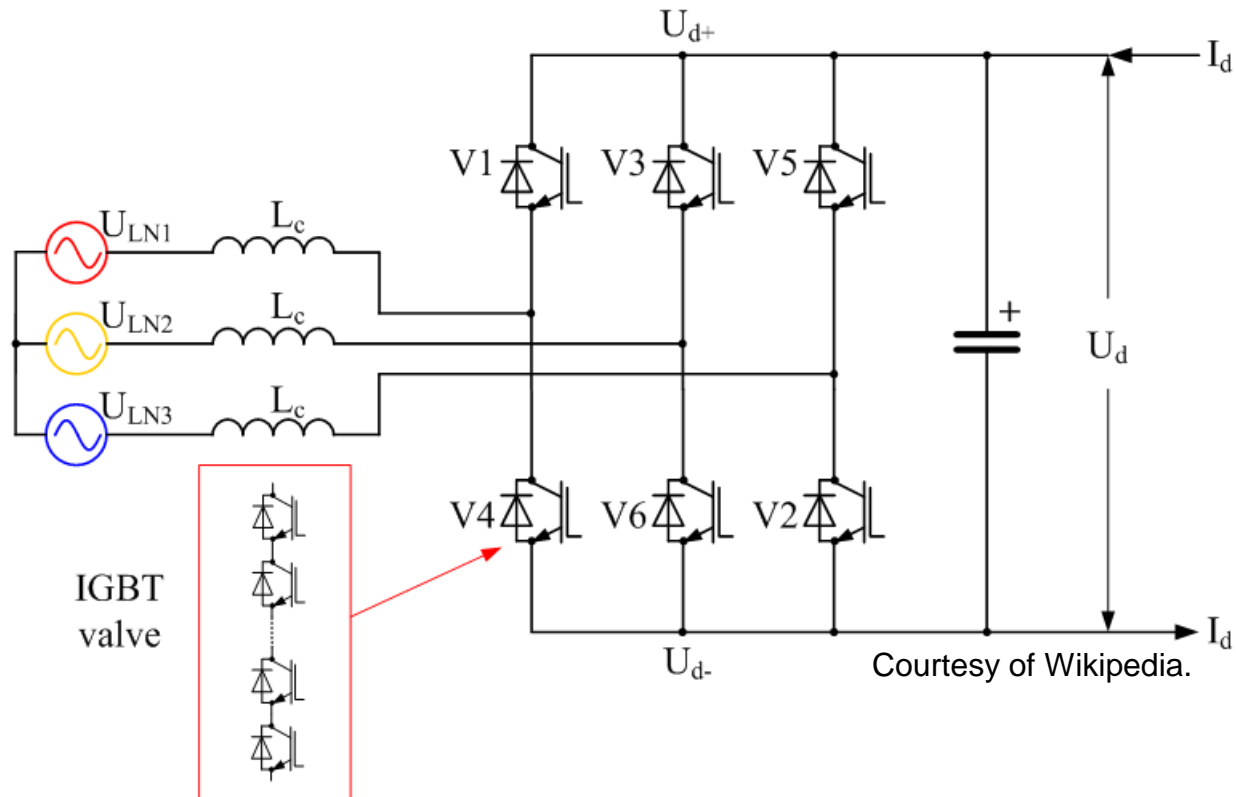


HVDC-VSC technology overview

■ Two level converters with series connected IGBTs

- Switching states

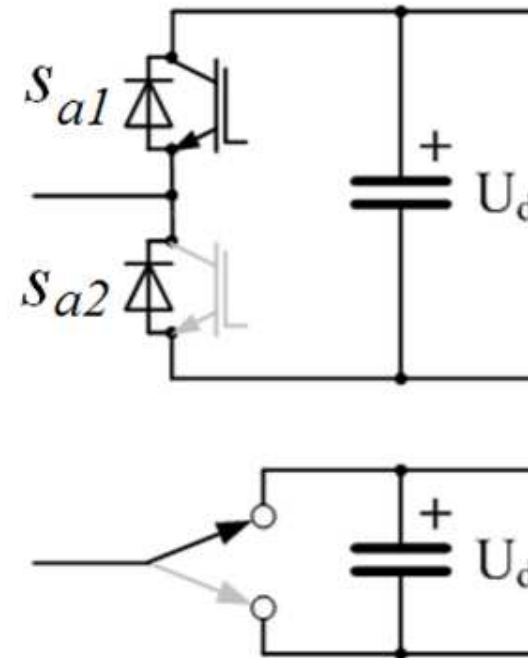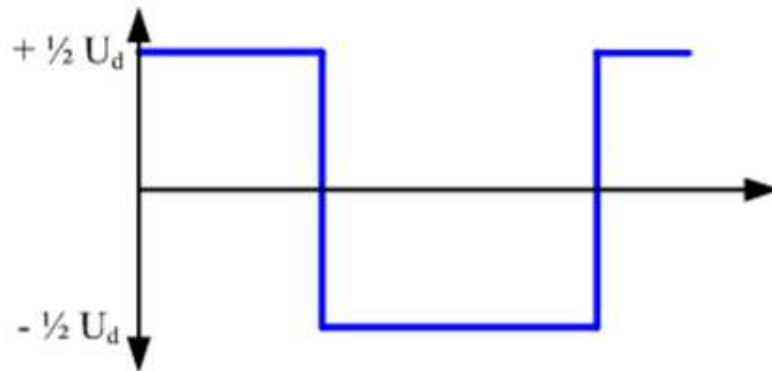S_{a1} ON S_{a2} OFF $\rightarrow v = v_{a0} = V_{dc}/2$





HVDC-VSC technology overview

■ Two level converters with series connected IGBTs

- Switching states

*S*_{a1} ON *S*_{a2} OFF → $v = v_{a0} = V_{dc}/2$

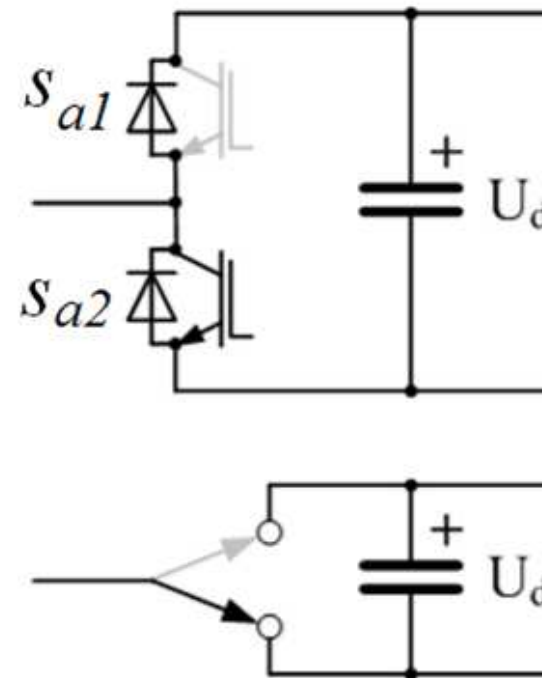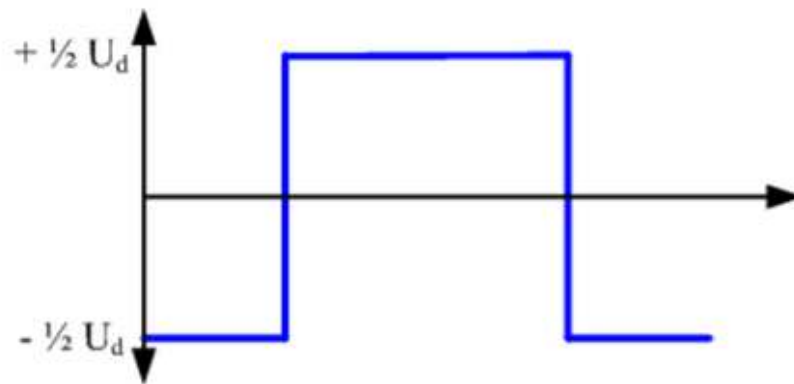*S*_{a1} OFF *S*_{a2} ON → $v = v_{a0} = -V_{dc}/2$





HVDC-VSC technology overview

■ Two level converters with series connected IGBTs

- Switching states


S_{a1} ON S_{a2} OFF $\rightarrow v = v_{a0} = V_{dc}/2$

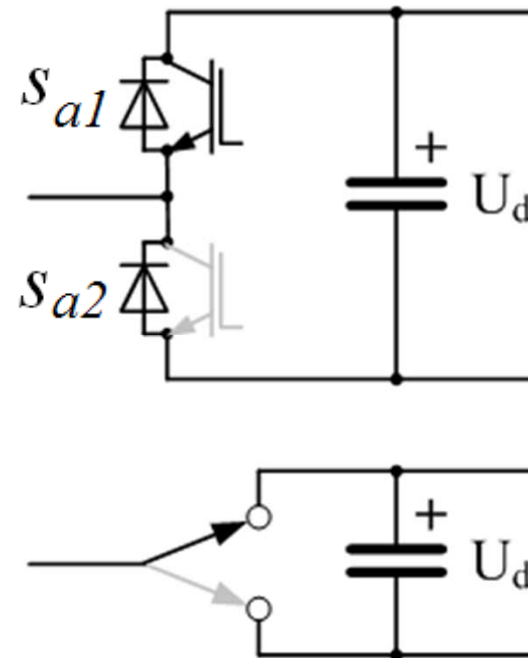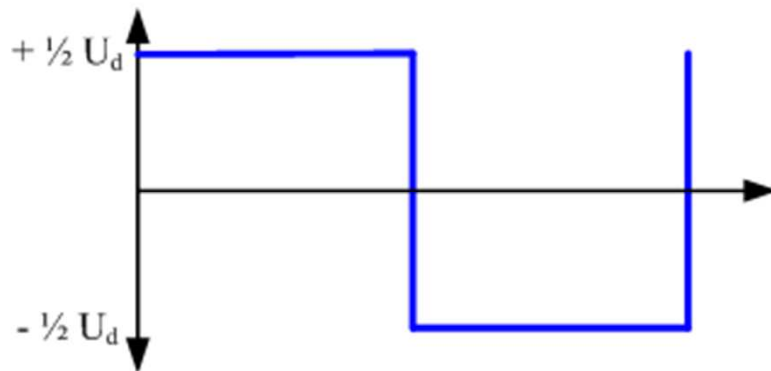S_{a1} OFF S_{a2} ON $\rightarrow v = v_{a0} = -V_{dc}/2$



HVDC-VSC technology overview

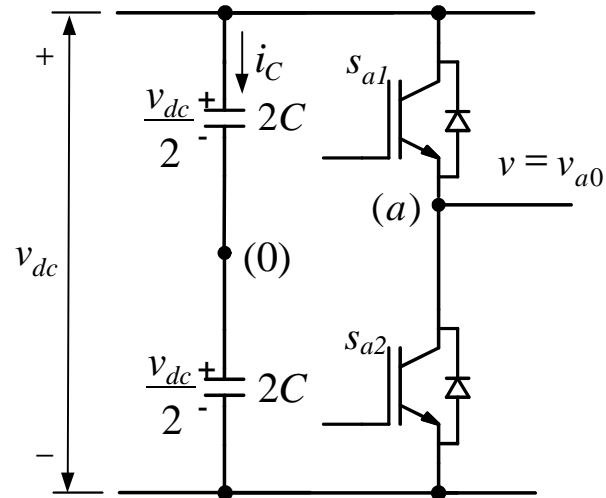Two level converters with series connected IGBTs. PWM modulation




Modulation signal:

$$v_s(t) = V_{SM} \sin \omega_s t$$

Output voltage:


If $v_s \geq v_T \rightarrow Sa1$ ON $Sa2$ OFF $\rightarrow v = v_{a0} = V_{dc}/2$

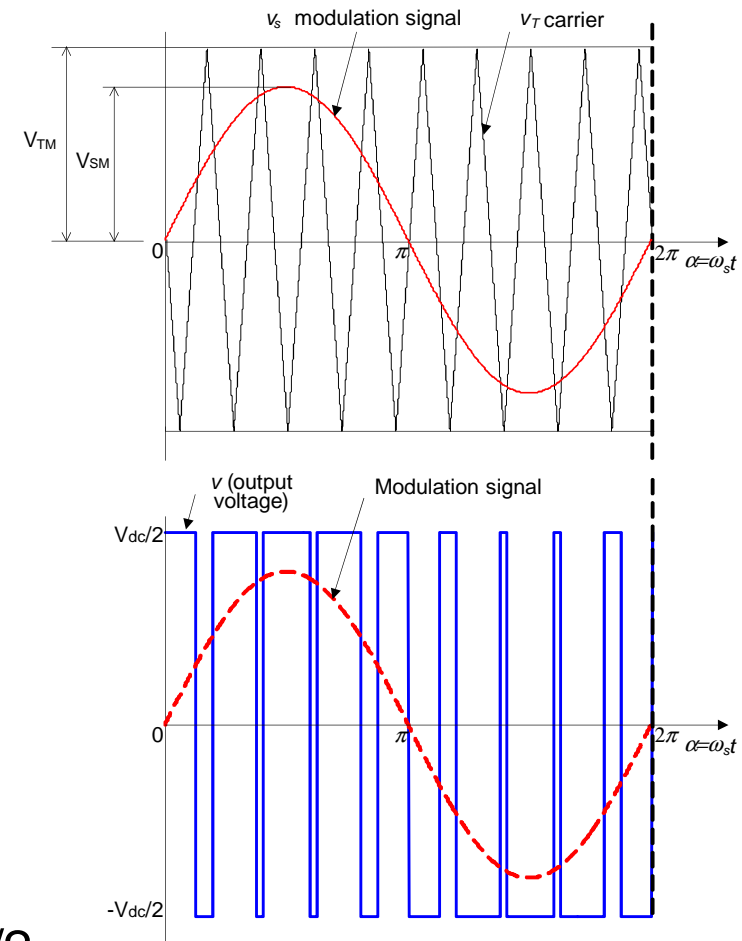If $v_s < v_T \rightarrow Sa1$ OFF $Sa2$ ON $\rightarrow v = v_{a0} = -V_{dc}/2$



HVDC-VSC technology overview

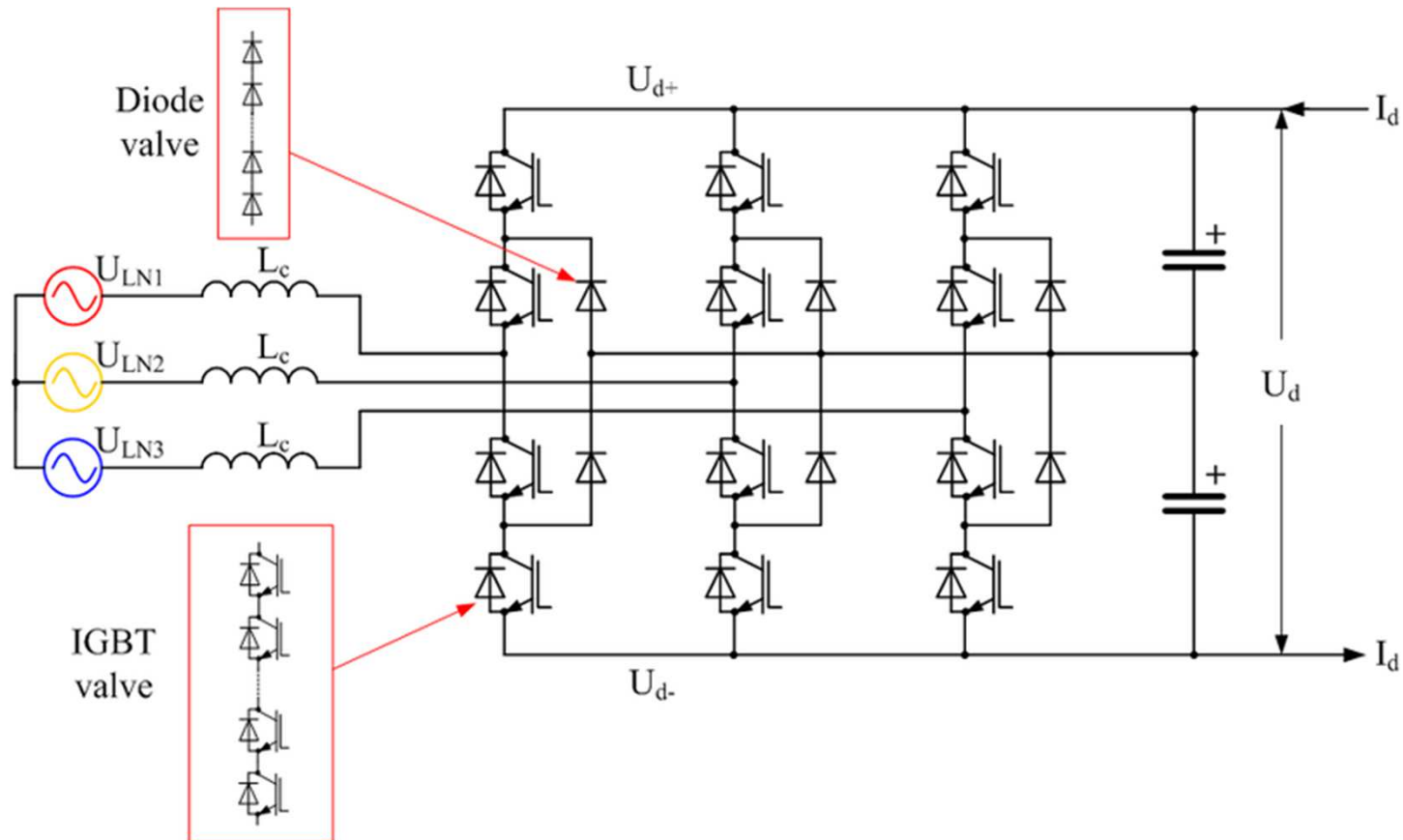- Three level NPC converters with series connected IGBTs
- ABB 2000-2005





HVDC-VSC technology overview

■ Three level NPC converters with series connected IGBTs

- Switching states

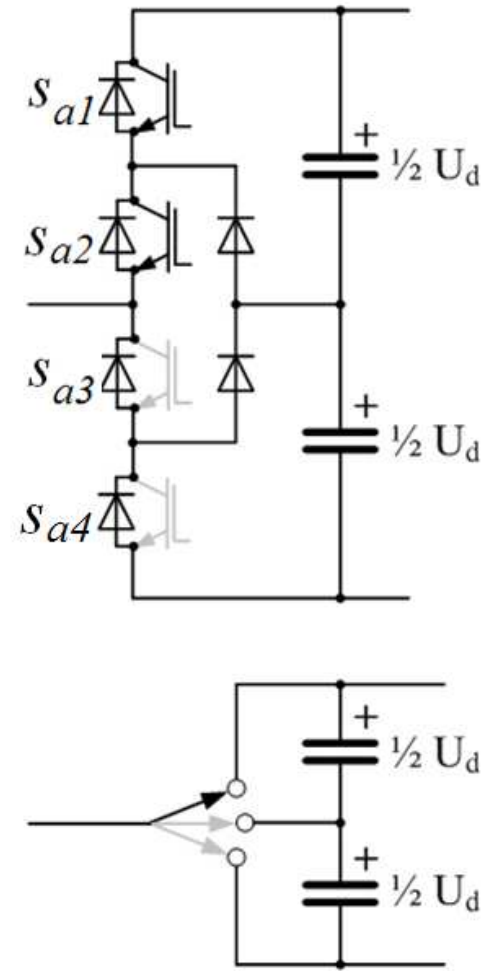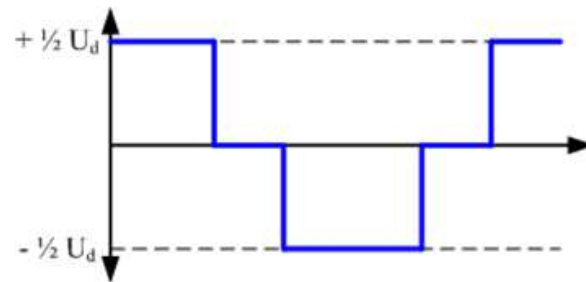S_{a1} ON S_{a2} ON S_{a3} OFF S_{a4} OFF $\rightarrow v_{a0} = U_{dc}/2$






HVDC-VSC technology overview

■ Three level NPC converters with series connected IGBTs

- Switching states

S_{a1} ON *S_{a2}* ON *S_{a3}* OFF *S_{a4}* OFF → $v_{a0} = U_{dc}/2$

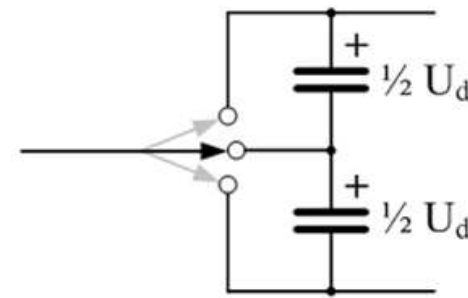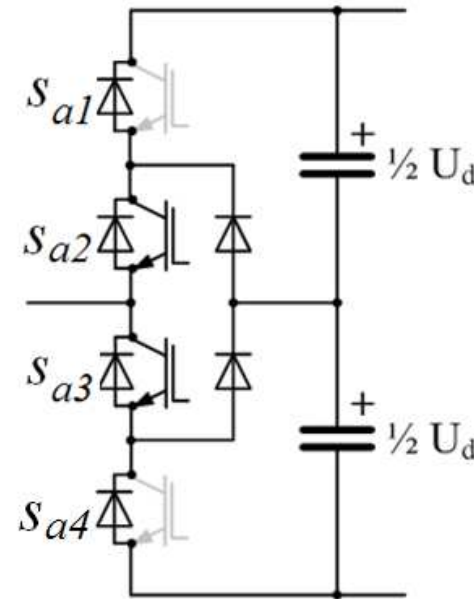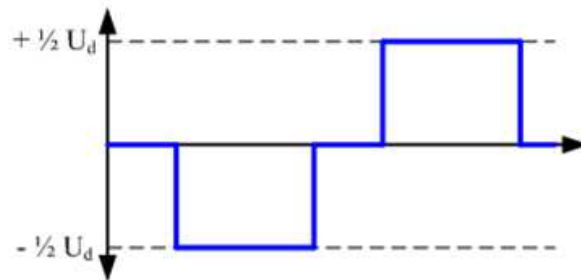S_{a1} OFF *S_{a2}* ON *S_{a3}* ON *S_{a4}* OFF → $v_{a0} = 0$



HVDC-VSC technology overview




■ Three level NPC converters with series connected IGBTs

- Switching states

*S*_{a1} ON *S*_{a2} ON *S*_{a3} OFF *S*_{a4} OFF → $v_{a0} = U_{dc}/2$

*S*_{a1} OFF *S*_{a2} ON *S*_{a3} ON *S*_{a4} OFF → $v_{a0} = 0$

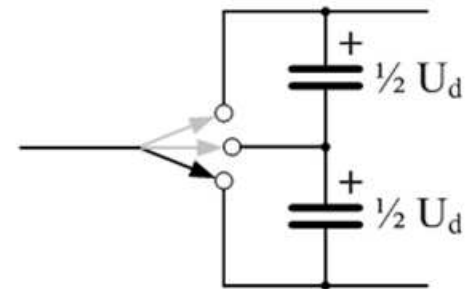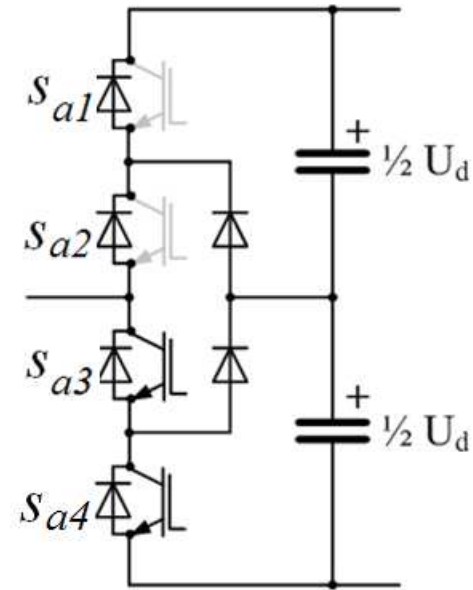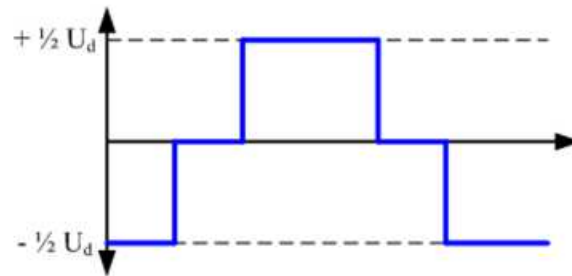*S*_{a1} OFF *S*_{a2} OFF *S*_{a3} ON *S*_{a4} ON → $v_{a0} = -U_{dc}/2$



HVDC-VSC technology overview



■ Three level NPC converters with series connected IGBTs

- Switching states

S_{a1} ON S_{a2} ON S_{a3} OFF S_{a4} OFF $\rightarrow v_{a0} = U_{dc}/2$



S_{a1} OFF S_{a2} ON S_{a3} ON S_{a4} OFF $\rightarrow v_{a0} = 0$

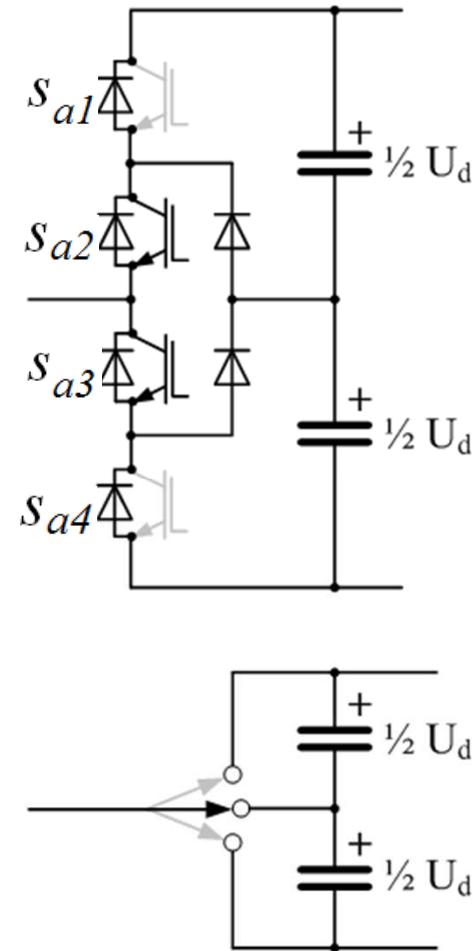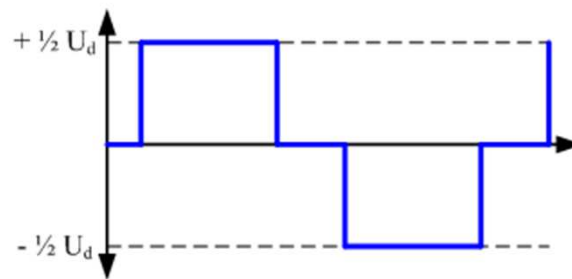S_{a1} OFF S_{a2} OFF S_{a3} ON S_{a4} ON $\rightarrow v_{a0} = -U_{dc}/2$



HVDC-VSC technology overview

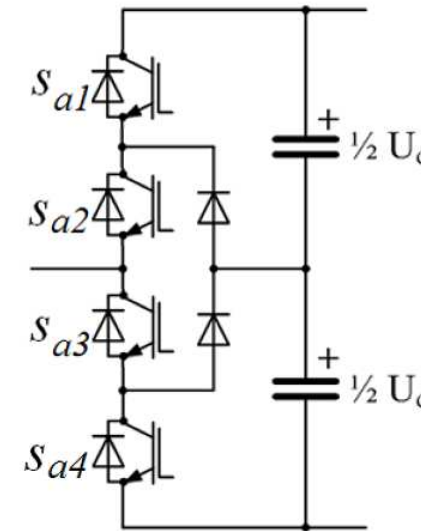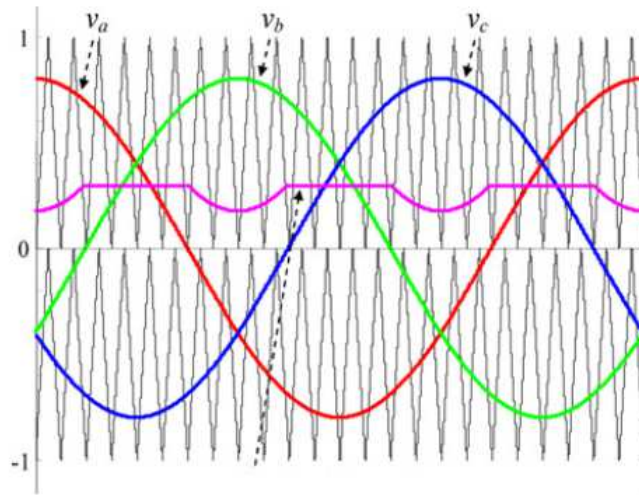■ Three level NPC converters with series connected IGBTs. PWM modulation.



Modulation signal

$$v_s(t) = V_{SM} \sin \omega_s t$$

Output voltage

if $v_s \geq 0$ and $v_s \geq v_{T1} \rightarrow S_{a1}$ ON S_{a2} ON S_{a3} OFF S_{a4} OFF $\rightarrow v = v_{a0} = U_d/2$



if $v_s \geq 0$ and $v_s < v_{T1} \rightarrow S_{a1}$ OFF S_{a2} ON S_{a3} ON S_{a4} OFF $\rightarrow v = v_{a0} = 0$

if $v_s < 0$ and $v_s \geq -v_{T2} \rightarrow S_{a1}$ OFF S_{a2} ON S_{a3} ON S_{a4} OFF $\rightarrow v = v_{a0} = 0$

if $v_s < 0$ and $v_s < -v_{T2} \rightarrow S_{a1}$ OFF S_{a2} OFF S_{a3} ON S_{a4} ON $\rightarrow v = v_{a0} = -U_d/2$

HVDC-VSC technology overview

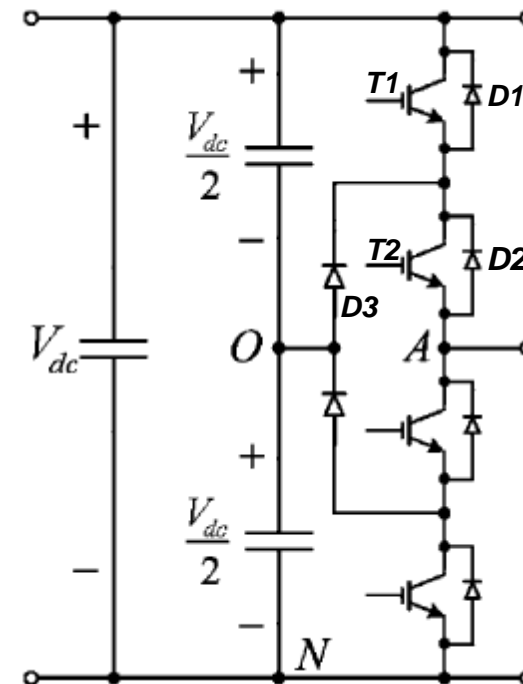
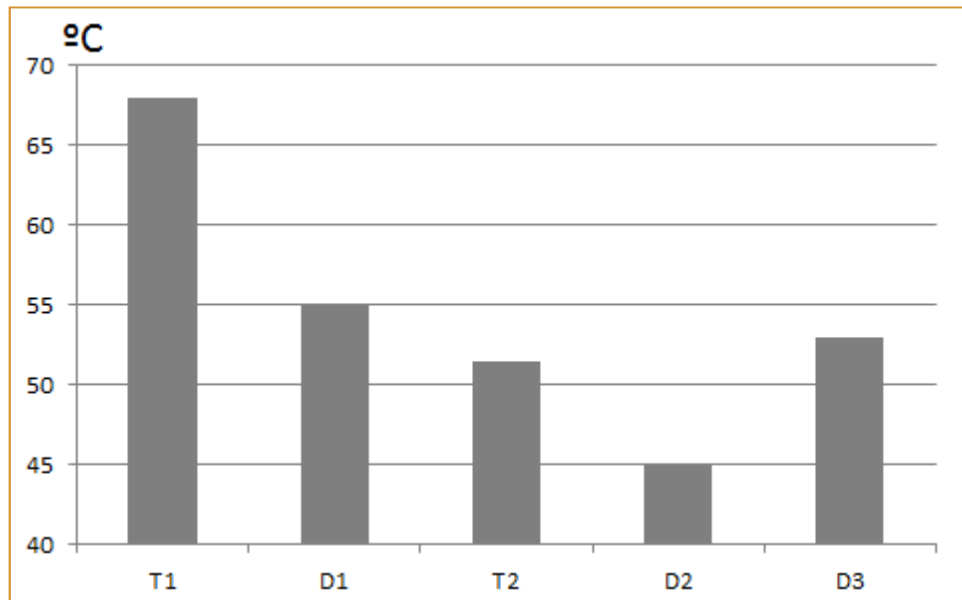
- Three level NPC converters with series connected IGBTs
 - Loss distribution



Uneven loss distribution between the switching devices. The converter needs to be overrated.

HVDC-VSC technology overview

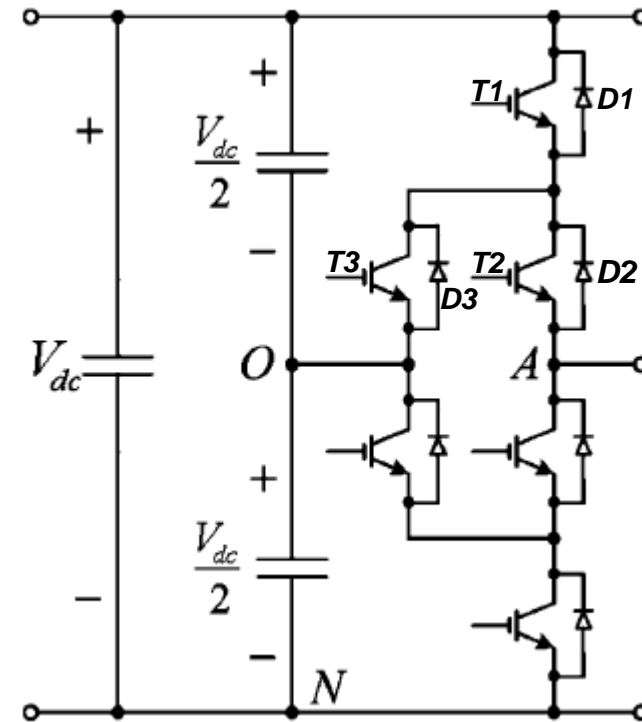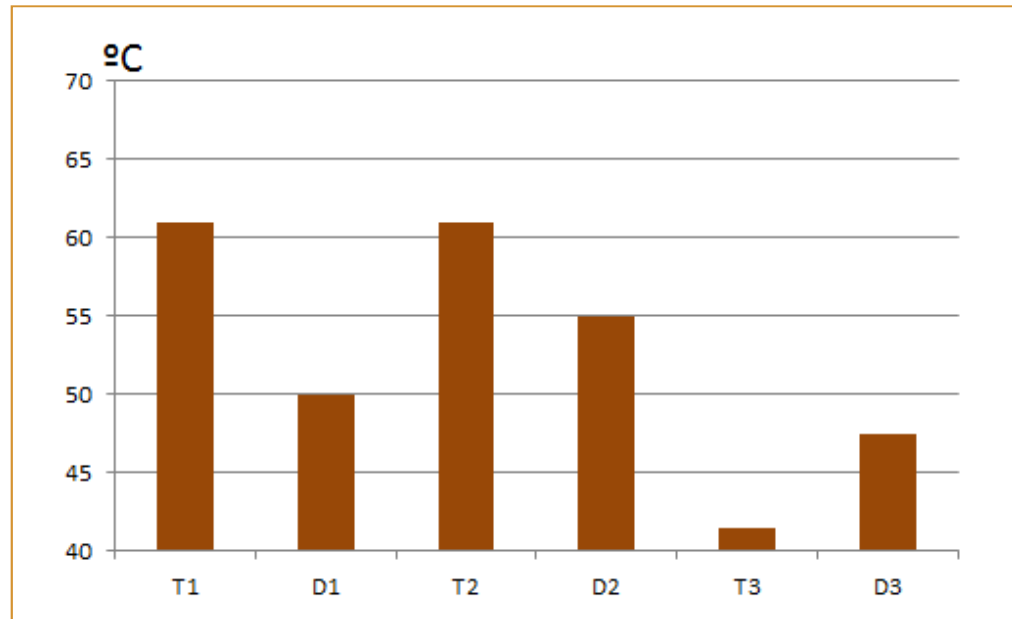
■ Three level Active NPC (ANPC) converters with series connected IGBTs



The ANPC introduces additional switching states that can be used to balance the power losses between semiconductor devices. Better converter use is achieved.

HVDC-VSC technology overview

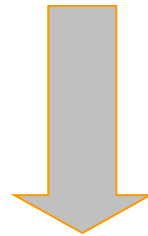
- Two and three level converters can facilitate AC/DC conversion in HVDC applications. However:
 - High switching frequency is mandatory due to the reduced number of levels .
 - Poor efficiency.
 - Direct connection of switching devices required.
 - Not easy scalable to higher power/voltage levels.



Modular Multilevel Converters MMC


HVDC-VSC technology overview

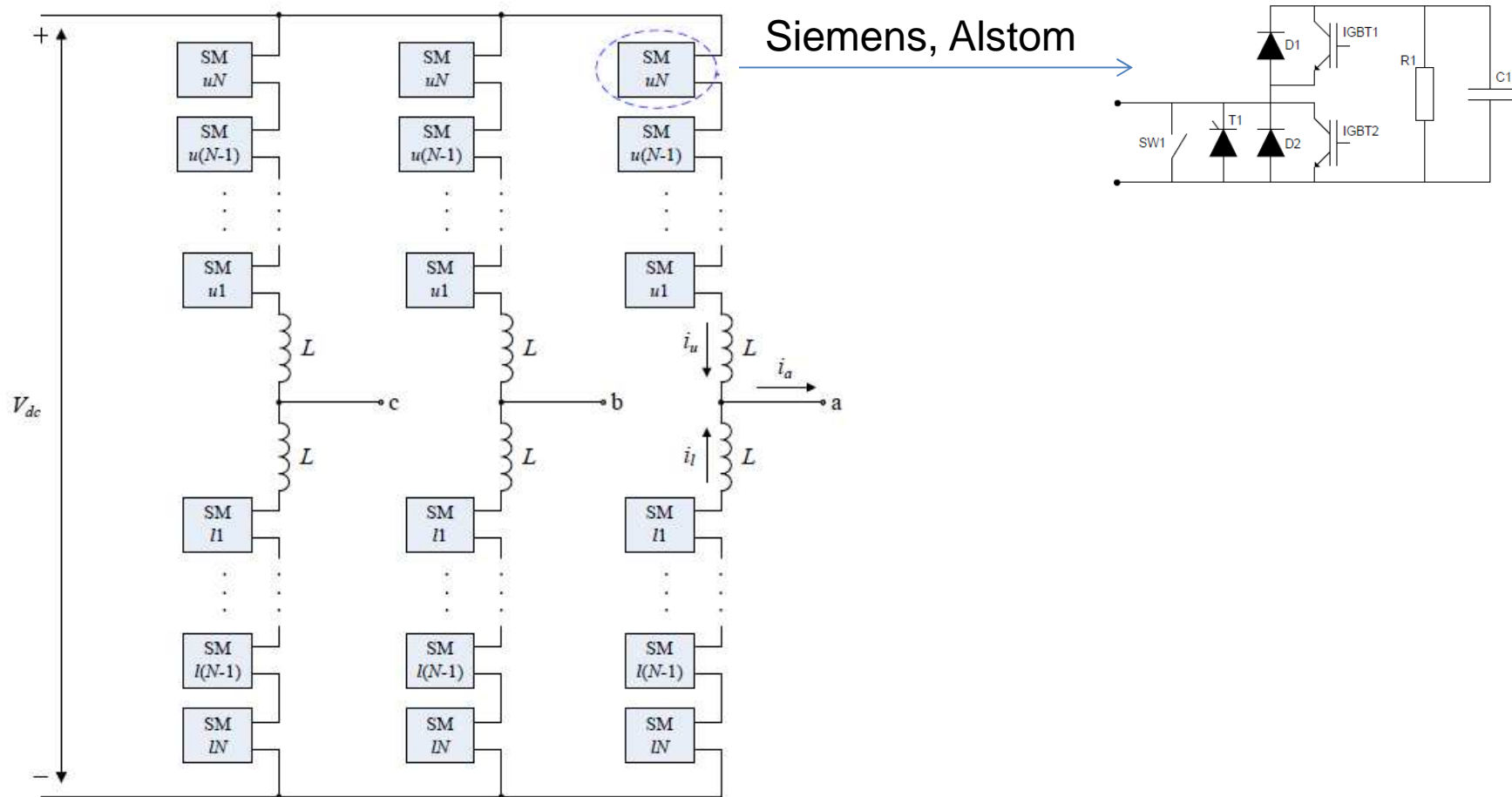- **Modular multilevel converters: Topology and manufacturers implementation**
 - Siemens 2007, ABB 2010, Alstom 2010




HVDC-VSC technology overview

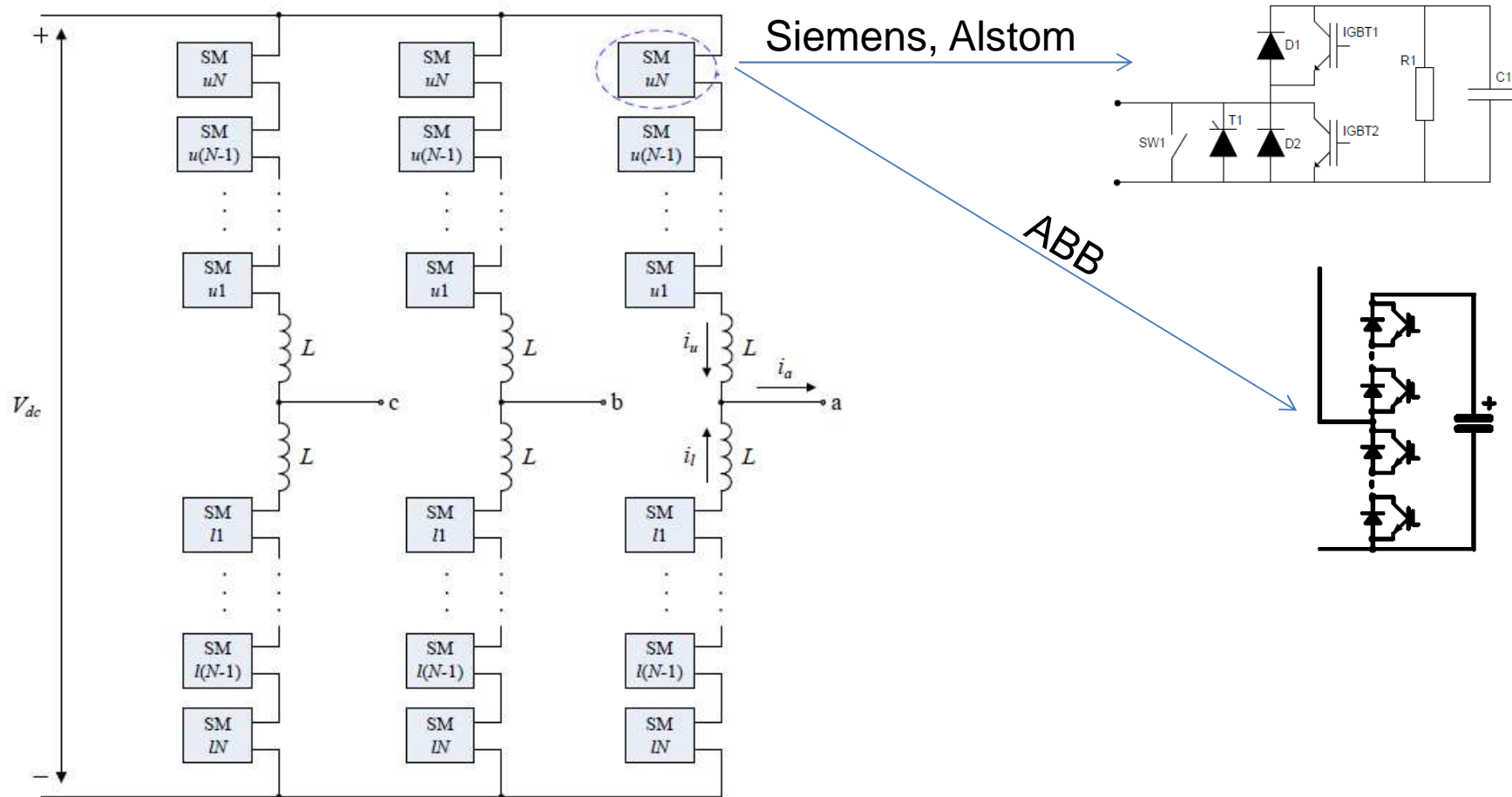- **Modular multilevel converters: Topology and manufacturers implementation**
 - Siemens 2007, ABB 2010, Alstom 2010







HVDC-VSC technology overview

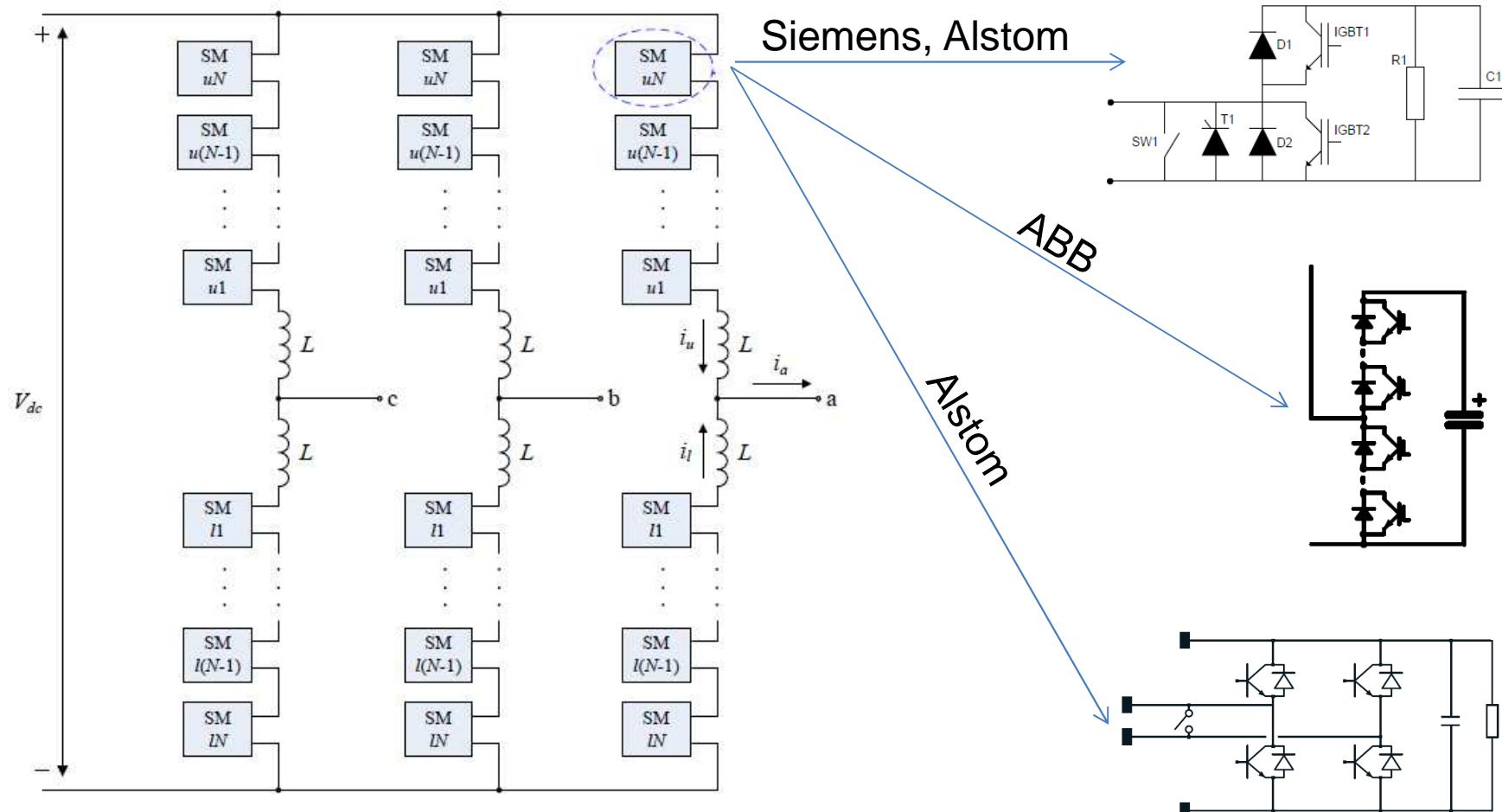- **Modular multilevel converters: Topology and manufacturers implementation**
 - Siemens 2007, ABB 2010, Alstom 2010




HVDC-VSC technology overview

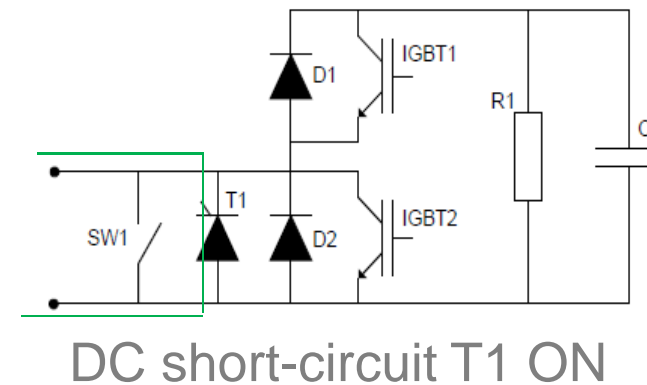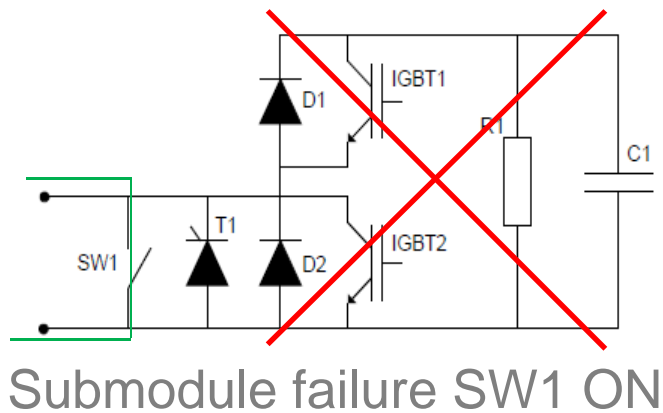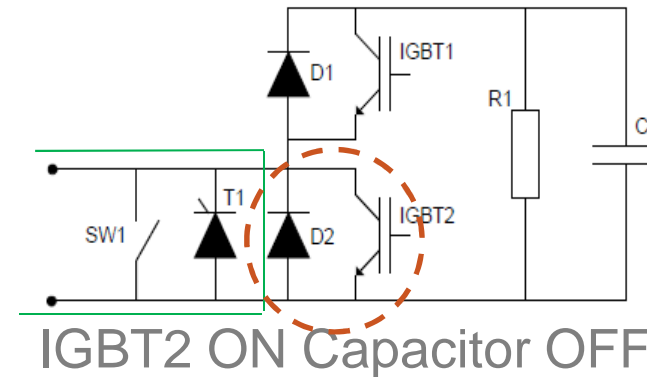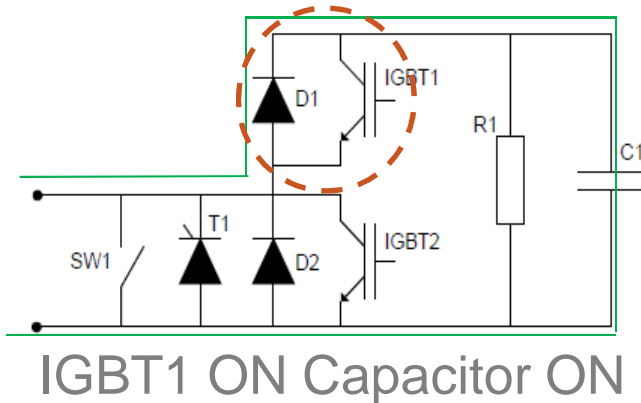■ Modular multilevel converters: Switching states



HVDC-VSC technology overview

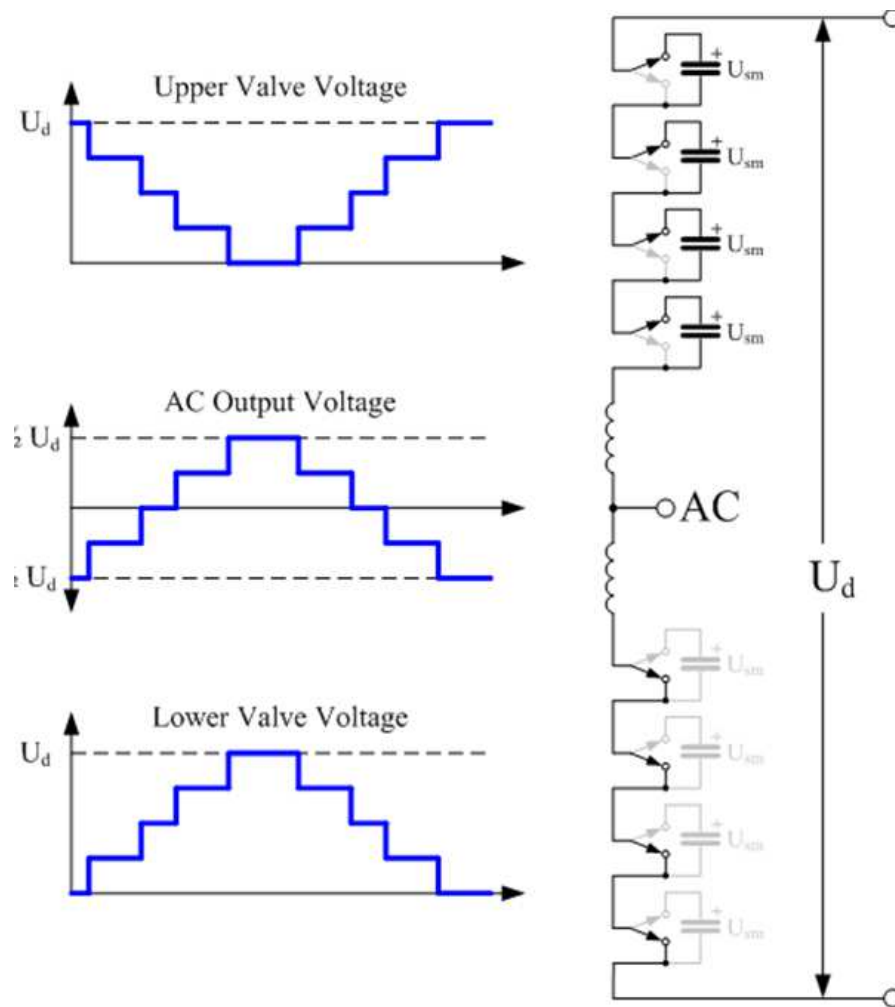
■ Modular multilevel converters: Switching states and commutation rules



- The number of activated submodules should be equal to n , being n the number of submodules in an arm.

HVDC-VSC technology overview

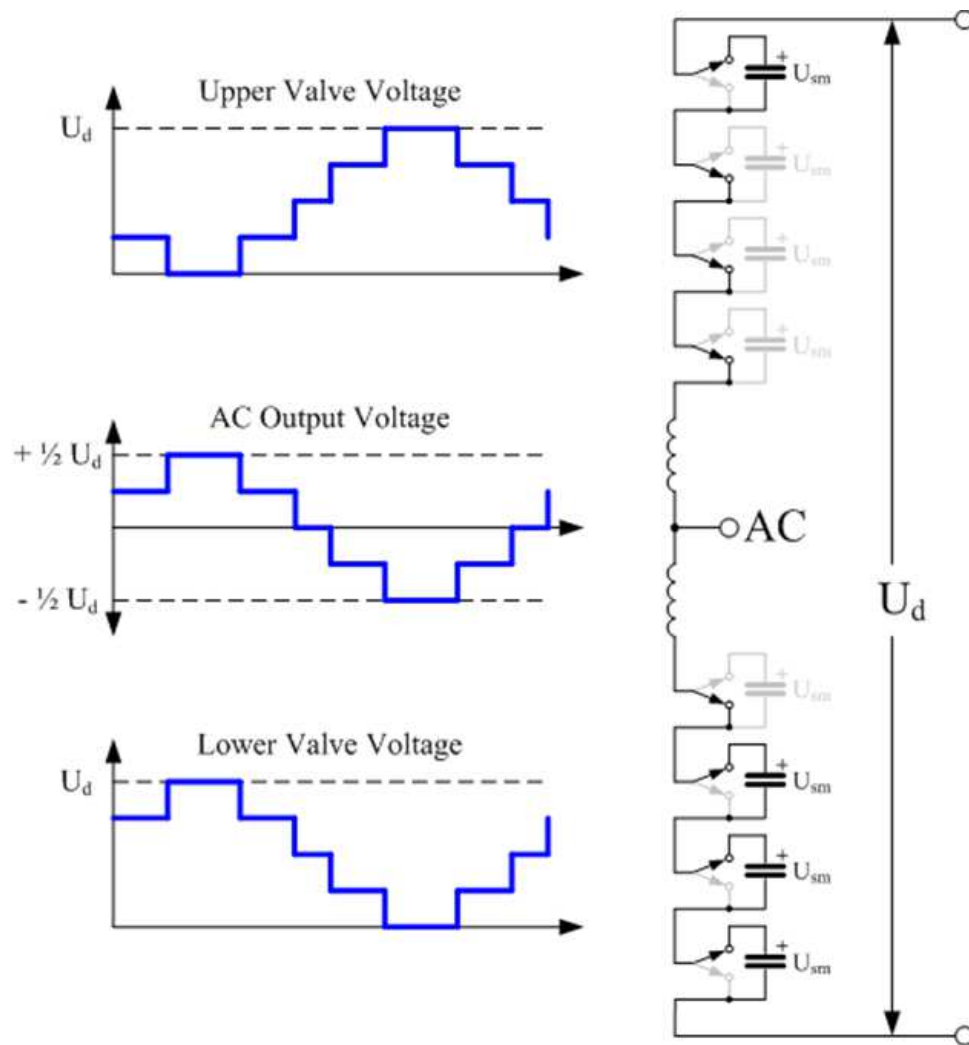
■ Modular multilevel converters: Switching states and commutation rules



- The number of activated submodules should be equal to n , being n the number of submodules in an arm.

HVDC-VSC technology overview

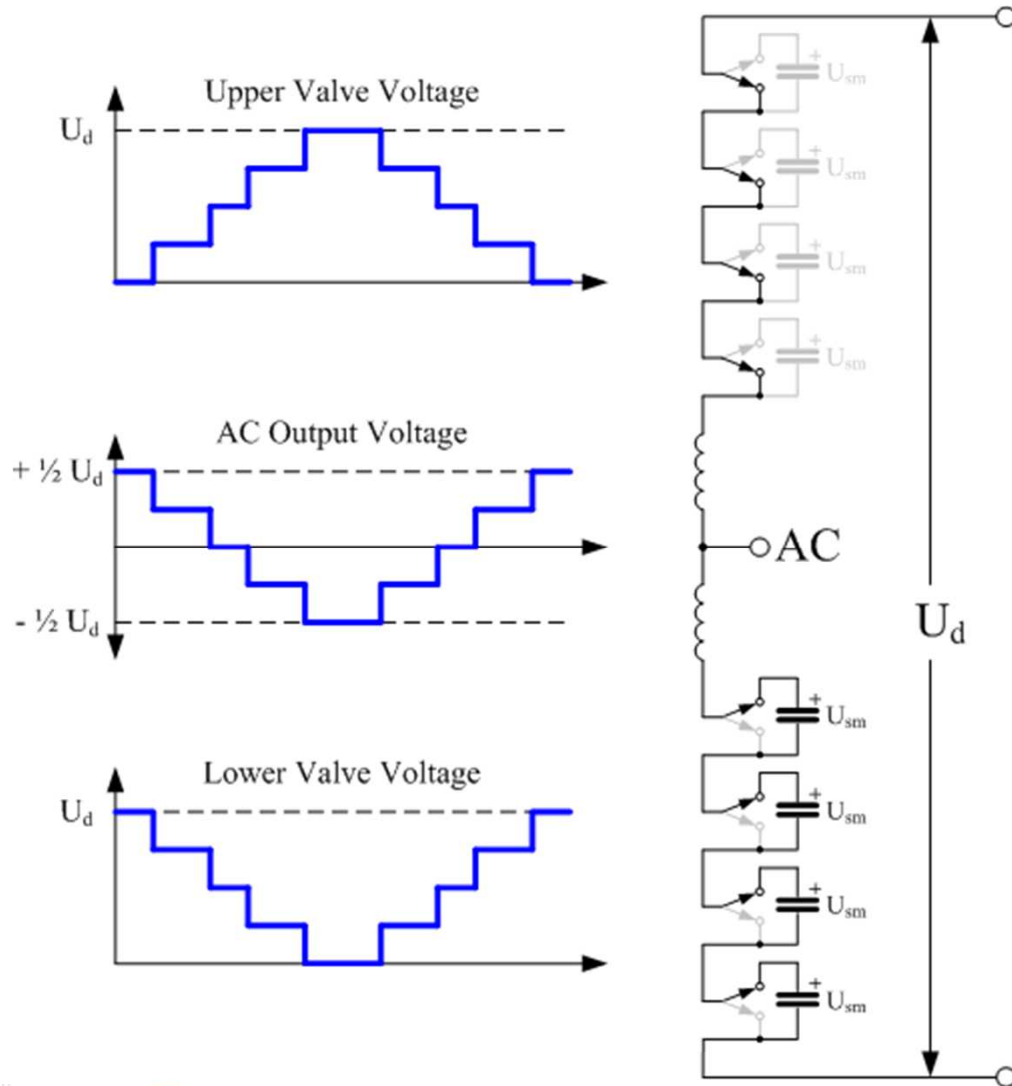■ Modular multilevel converters: Switching states and commutation rules



Advantages:


- Low switching frequency
- High efficiency (around 99%)
- Easily scalable
- Low harmonic distortion

Disadvantages:

- Requires twice the number of semiconductors than a two level converter and heavier capacitors.
- Complex control

HVDC-VSC technology overview

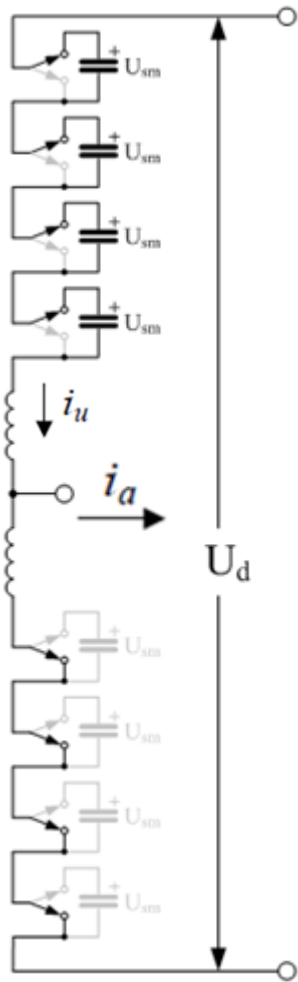■ Modular multilevel converters: Equivalent circuit



To maintain the charge in the capacitors stable a dc current has to be added to the arm currents.


$$i_u = \frac{i_a}{2} + i_{dc}$$

It can be demonstrated that the dc current needed to maintain stable the capacitors voltage is given by the following expression:


$$i_{dc} = \frac{v_{ac} i_a \cos \phi}{2U_d}$$

HVDC-VSC technology overview


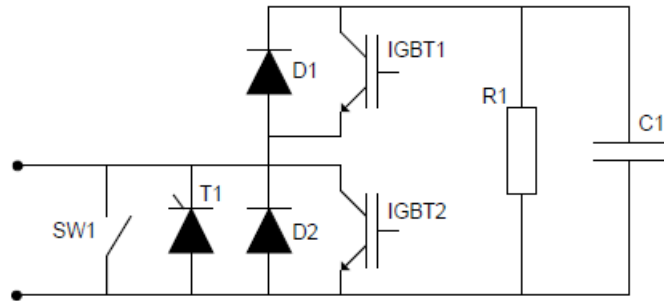
■ Modular multilevel converters: Manufacturers implementations



ALSTOM

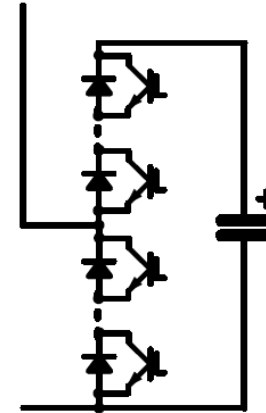

ABB

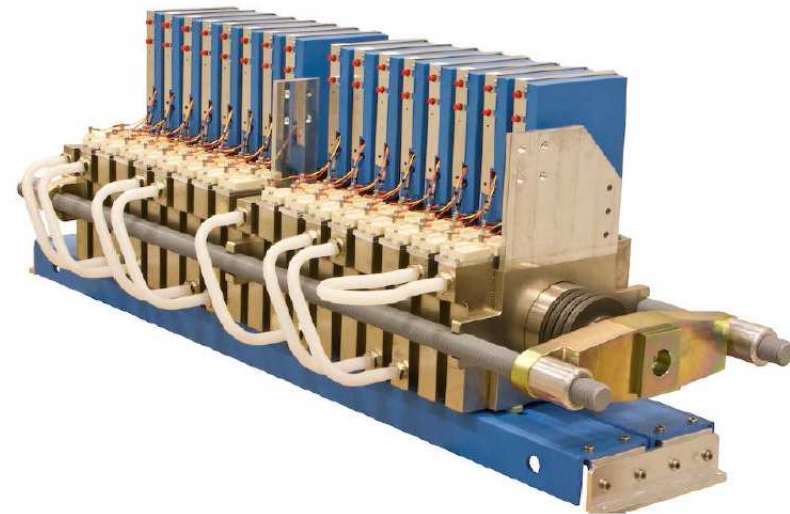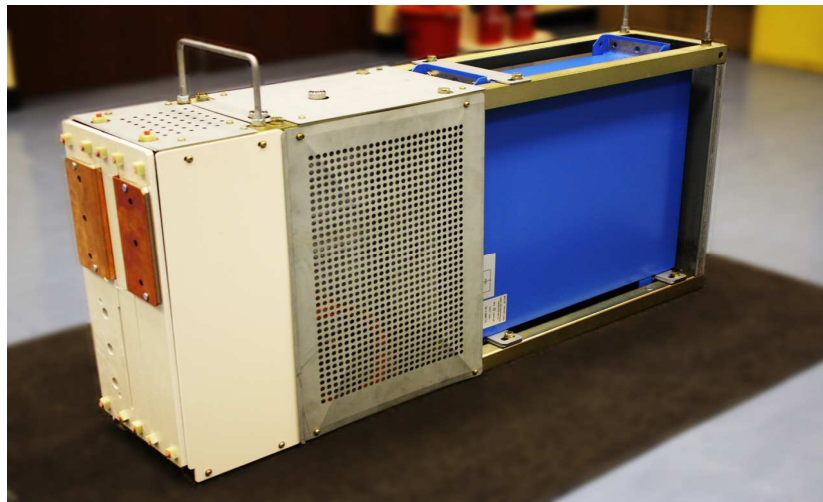

HVDC-VSC technology overview

■ Modular multilevel converters: Manufacturers implementations

Alstom implementation



Introduction

Transmission layouts for OWPP

HVDC-VSC technology overview

- Two level converters.
- Three level NPC converters
- Modular multilevel converters

Conclusions

Conclusions

- This presentation has described the current commercial available solutions for energy transmission of offshore wind farms
- For large offshore wind power farms located far from the PCC the most suitable energy transmission layout is based on HVDC-VSC technologies.
- The MMC represents a really important milestone in the evolution of HVDC-VSC transmission links.
- Future research topics
 - New energy transmission layouts with MVDC collector systems.
 - New converter topologies for HVDC-VSC transmission systems.
 - Development of control algorithms for multiterminal HVDC links.

www.tecnalia.com

Thank you for your
attention!

tecnalia  Inspiring
Business